



# Digital Logic :

Coming Back to our main Topic :

Boolean Algebra

Website : <https://www.goclasses.in/>

# Introduction

- Boolean Algebra is used to analyze and simplify the digital (logic) circuits.
- It uses only the binary numbers i.e. 0 and 1. It is also called as **Binary Algebra** or **logical Algebra**.
- It is a convenient way and systematic way of expressing and analyzing the operation of logic circuits
- Boolean algebra was invented by **George Boole** in 1854.





## Introduction

- Variable used in Boolean algebra can have only two values. Binary 1 for HIGH and Binary 0 for LOW.
- Complement of a variable is represented by an overbar (-). Thus, complement of variable B is represented as  $B'$ . Thus if  $B = 0$  then  $B' = 1$  and if  $B = 1$  then  $B' = 0$ .
- ORing of the variables is represented by a plus (+) sign between them. For example ORing of A, B, C is represented as  $A + B + C$ .
- Logical ANDing of the two or more variable is represented by writing a dot between them such as  $A \cdot B \cdot C$ . Sometime the dot may be omitted like ABC.

# Boolean Operations

AND

A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

OR


A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

Complement +  
Not


A	A'
0	1
1	0

## Two Basic Functions

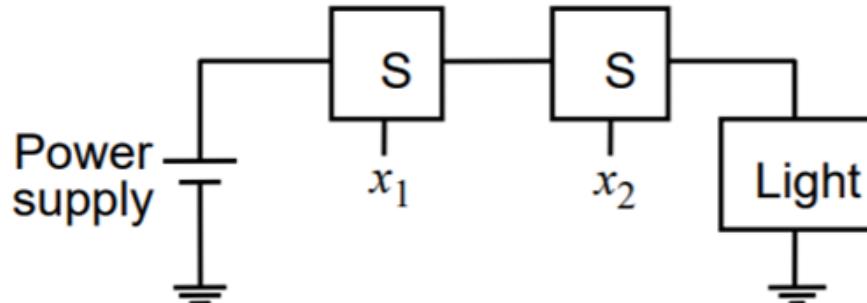(a) The logical AND function  
(series connection)



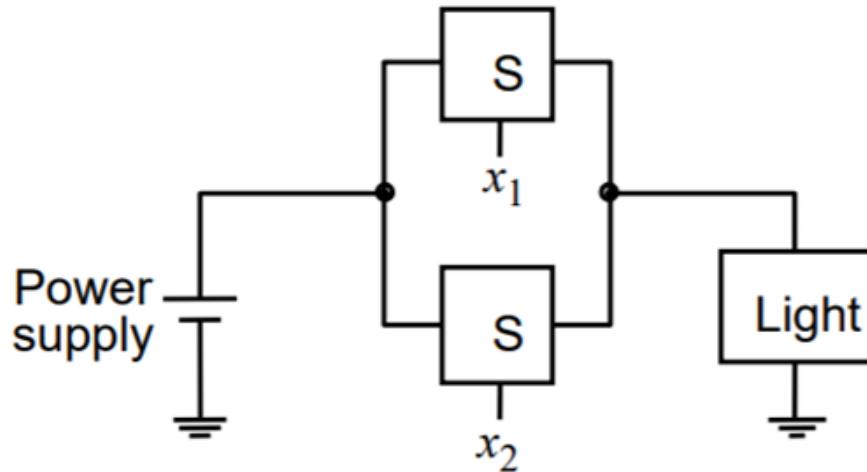(b) The logical OR function  
(parallel connection)



## Boolean Logic

- Binary digits (or bits) have two values: {1,0}
- All logical functions can be implemented in terms of three logical operations:

NOT

x	$\bar{x}$
0	1
1	0

AND

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

OR

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1



The complement of 0 is 1, and the complement of 1 is 0. Symbolically, we write

$$0' = 1 \quad \text{and} \quad 1' = 0$$






If  $X$  is a switching variable,

$$X' = 1 \text{ if } X = 0 \quad \text{and} \quad X' = 0 \text{ if } X = 1$$

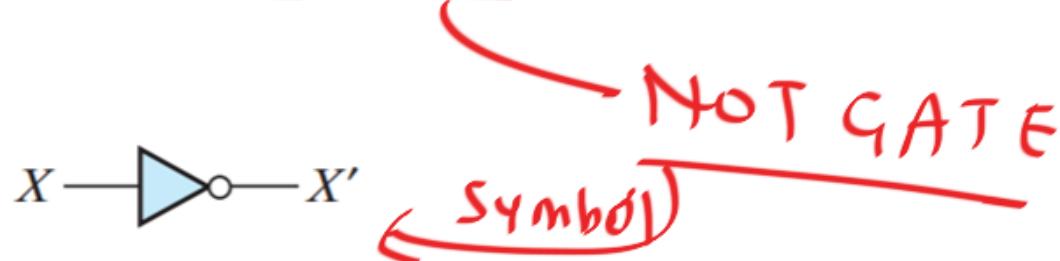
An alternate name for complementation is inversion, and the electronic circuit which forms the inverse of  $X$  is referred to as an inverter. Symbolically, we represent an inverter by



where the circle at the output indicates inversion. A low voltage at the inverter input produces a high voltage at the output and vice versa.




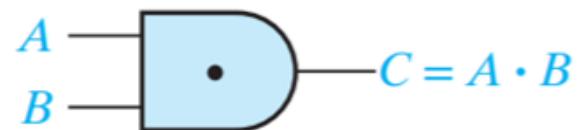A logic gate which performs the AND operation is represented by



The gate output is  $C = 1$  if and only if the gate inputs  $A = 1$  and  $B = 1$ .

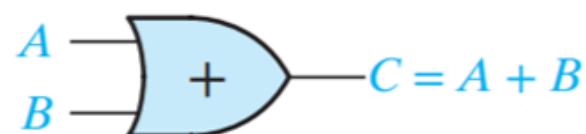A logic gate which performs the OR operation is represented by



The gate output is  $C = 1$  if and only if the gate inputs  $A = 1$  or  $B = 1$  (or both).



## Digital Logic :

Next Topic :

More Standard Boolean Operations

NAND, NOR, ExOR, ExNOR



NAND operation:

Symbol:  $\uparrow$

$$\underbrace{a \uparrow b}_{=} = \overline{\underline{ab}}$$

N A ND  
           
    ↓

Not of AND



NOR Operation:

Symbol:  $\downarrow$

$$\{ \downarrow \} = \overline{a+b}$$

N OR  
↓

NOT of OR

Truth Table:

	a	b	$a \uparrow b = \overline{ab}$	$a+b$	$a \downarrow b = \overline{a+b}$	
Row 1	0	0	1	0	1	0
Row 2	0	1	1	1	0	1
Row 3	1	0	1	1	0	0
Row 4	1	1	0	1	0	0

Universal gates: NAND, NOR


Will see  
Later

x	y	$z = \overline{xy}$
0	0	1
0	1	1
1	0	1
1	1	0

NAND = AND



x	y	$z = \overline{x+y}$
0	0	1
0	1	0
1	0	0
1	1	0

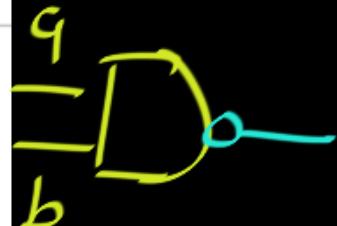




## Operation

$$\overline{a \uparrow b} = \overline{\overline{a} b}$$

$$a \downarrow b = \overline{a + b}$$

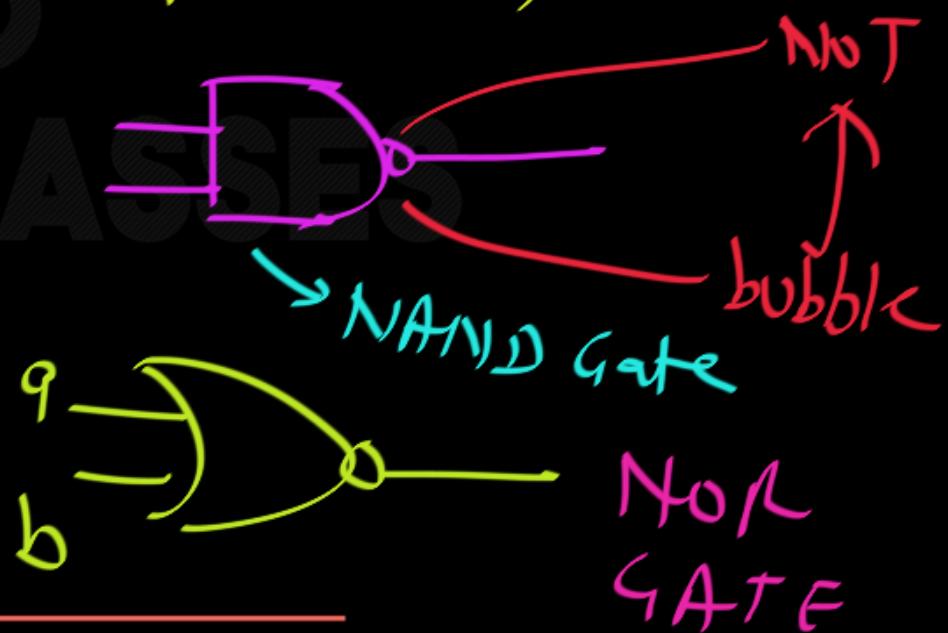Digital CKT ✓  
implementing that  
operation



## Exclusive OR (ExOR)

Symbol:  $\oplus$

Exclusively one of the variable  
must be 1.

Analogy:  
Exclusive news

a	b	$a \oplus b$
0	0	0
0	1	1
1	0	1
1	1	0



# Digital Logic

$$a \oplus b = 1$$

iff

$$a \neq b$$

~~xx~~  
=

$$0 \oplus 1 = 1$$

$$1 \oplus 0 = 1$$

$$1 \oplus 1 = 0$$

$$0 \oplus 0 = 0$$

Convention while writing Expression :

$$\underline{a = 0} \equiv \overline{a}$$

$$\begin{array}{l} \underline{\underline{a = 1}} \\ \overline{a} = 0 \end{array} \equiv a$$

Explain later

$$a = 0 \equiv a'$$

$$a = 1 \equiv a$$

# Exclusive-OR and Equivalence Operations

The *exclusive-OR* operation ( $\oplus$ ) is defined as follows:

$$\begin{array}{ll} 0 \oplus 0 = 0 & 0 \oplus 1 = 1 \\ 1 \oplus 0 = 1 & 1 \oplus 1 = 0 \end{array}$$

The truth table for  $X \oplus Y$  is

$X$	$Y$	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

From this table, we can see that  $X \oplus Y = 1$  iff  $X = 1$  or  $Y = 1$ , but *not* both. The ordinary OR operation, which we have previously defined, is sometimes called inclusive OR because  $X + Y = 1$  iff  $X = 1$  or  $Y = 1$ , or both.

a	b	$a \oplus b$
0	0	0
1	0	1
0	1	1
1	1	0

$$a \oplus b = 1$$

iff

$$\underline{a=0, b=1}$$



$$\underline{a=1, b=0}$$

$$a \oplus b = \bar{a}b + a\bar{b}$$

ExNor = Complement of ExOR

Symbol:  $\odot$ ,  $\Leftrightarrow$

a	b	$a \oplus b$	$a \odot b \equiv a \Leftrightarrow b$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1



$$a \odot b = 1 \text{ iff } \underline{\underline{a=b}}$$

$$a \Leftrightarrow b = 1 \text{ iff } a=b$$



$$a \oplus b = 1 \quad \text{iff} \quad [a \neq b]$$

$$a \odot b = 1 \quad \text{iff} \quad [a = b]$$

Complement

$$\overline{a \oplus b} = a \odot b$$




Exclusive OR can be expressed in terms of AND and OR. Because  $X \oplus Y = 1$  iff  $X$  is 0 and  $Y$  is 1 or  $X$  is 1 and  $Y$  is 0, we can write

$$X \oplus Y = X'Y + XY' \quad (3-6)$$

The first term in (3-6) is 1 if  $X = 0$  and  $Y = 1$ ; the second term is 1 if  $X = 1$  and  $Y = 0$ .

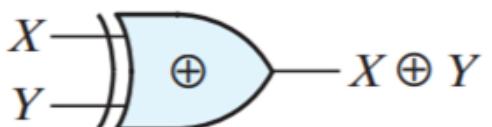We will use the following symbol for an exclusive-OR gate:







## Operations :

Exor }  
 $a \oplus b$

ExNor  
 $a \ominus b$

## Digital Ckt

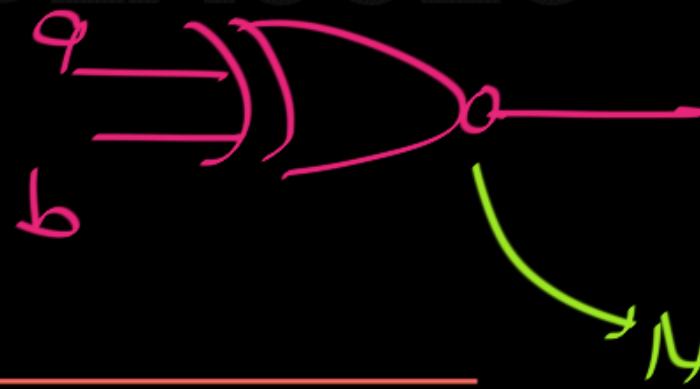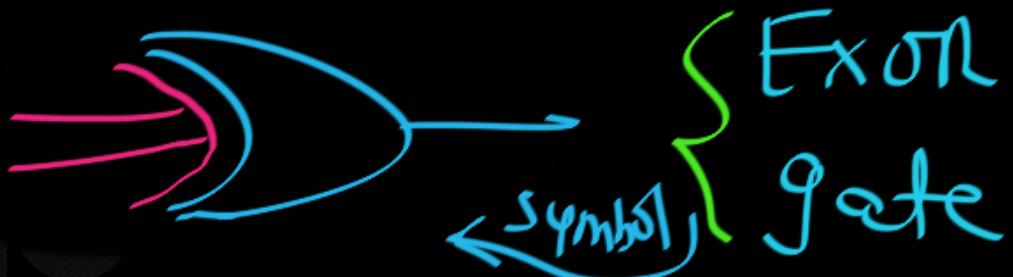

The *equivalence* operation ( $\equiv$ ) is defined by

$$\begin{array}{ll} (0 \equiv 0) = 1 & (0 \equiv 1) = 0 \\ (1 \equiv 0) = 0 & (1 \equiv 1) = 1 \end{array} \quad (3-16)$$

The truth table for  $X \equiv Y$  is

$X$	$Y$	$X \equiv Y$
0	0	1
0	1	0
1	0	0
1	1	1

From the definition of equivalence, we see that  $(X \equiv Y) = 1$  iff  $X = Y$ . Because  $(X \equiv Y) = 1$  iff  $X = Y = 1$  or  $X = Y = 0$ , we can write

$$(X \equiv Y) = XY + X'Y' \quad (3-17)$$



a	b	$a \oplus b$
0	0	1
0	1	0
1	0	0
1	1	1

$a \oplus b = 1$  iff

$a=0, b=1$  OR  $a=1, b=0$

$$a \oplus b = \overline{a} \overline{b} + ab$$

write equation ✓




a	b	f(a,b)
0	0	1
0	1	0
1	0	0
1	1	1

Write equation for f:

$$f = \overline{\underline{a}} \overline{\underline{b}} + \underline{\overline{a}} \overline{\underline{b}} + \underline{a} \underline{\overline{b}}$$



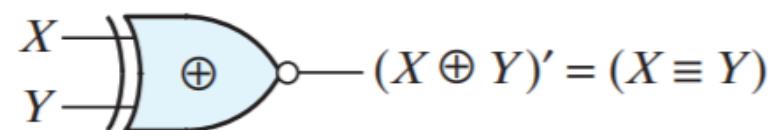Because equivalence is the complement of exclusive OR, an alternate symbol for the equivalence gate is an exclusive-OR gate with a complemented output:



The equivalence gate is also called an exclusive-NOR gate.





# Boolean Algebra :

Next Topic :

Boolean Expressions and Truth Table  
(Standard form of Truth Table)

a	b	ab
1	0	0 ✓
1	1	1 ✓
0	1	0 ✓
0	0	0 ✓

Truth Table ✓

Standard form of  
Truth Table

Row Number	a	b	ab
0	0	0	0
1	0	1	0
2	1	0	0
3	1	1	1

	a	b	c	$(\underline{a+b}) \cdot c = E$
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1

NOTE:

When  $c=0$



then  $E=0$

When  $c=1$

$$E = (\underline{a+b})$$



AND GATE:

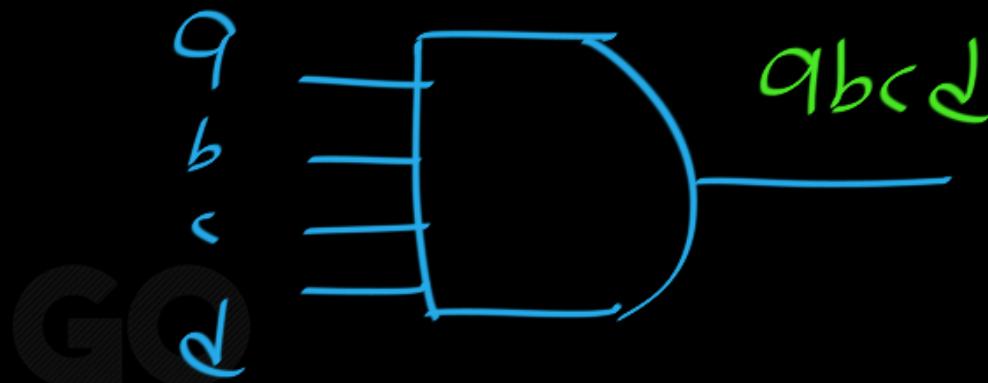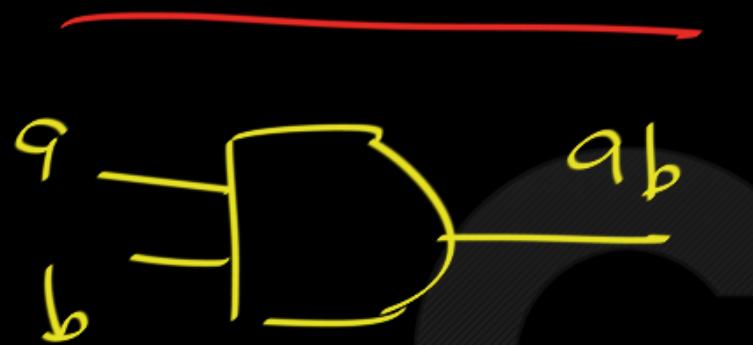

GO  
CLASSES



## Truth Table of 3-Input AND and OR Operations

Row #

Row #	$x_1$	$x_2$	$x_3$	$x_1 \bullet x_2 \bullet x_3$	$x_1 + x_2 + x_3$
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	0	1
4	1	0	0	0	1
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1

## Symbols

- AND



- Dot ( • )
  - Imagine it to be like multiplication
  - Example  $x \bullet y$
  - Called “x and y”

- OR

- Plus ( + )
  - Imagine it to be like addition
  - Example  $x + y$
  - Called “x or y”

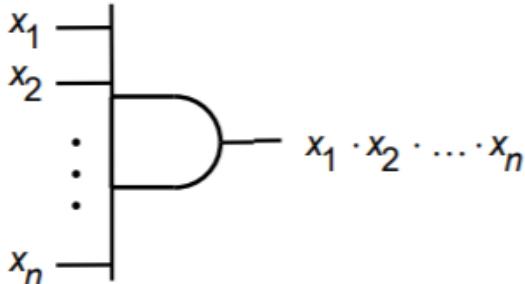
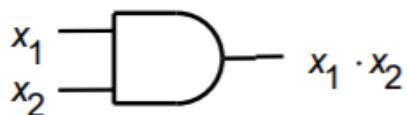
## NOT Operation

- Symbol
  - Closing single quote '
  - Also overline  $\bar{x}$  and ! symbol
  - Example:  $x'$ ,  $\bar{x}$ ,  $\bar{!x}$
- Calling
  - $x$  complement
  - “not of  $x$ ”
  - Simpler: “ $x$  bar”




(a) AND gates

## Symbols

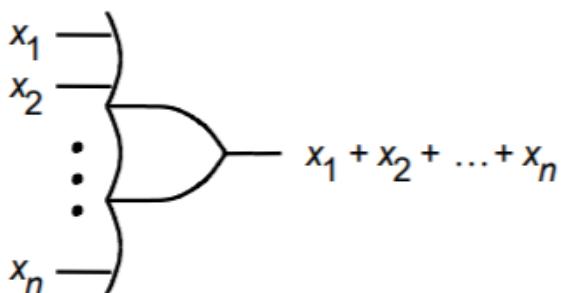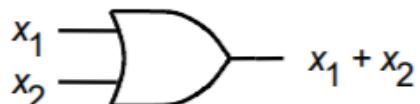

(b) OR gates

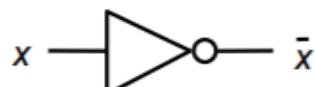

(c) NOT gate



# Literal:

"Each appearance of a variable or its complement in an expression will be referred to as a literal. Thus, the following expression, which has three variables, has 10 literals:

$$ab'c + a'b + a'bc' + b'c'$$

Variable =  $a$

Literal =  $a, \bar{a}$



$$E = \underbrace{a + a + a}$$

#variables = 1

# literals = 3

$$= a + \bar{a} + ab$$

$\Rightarrow$  #variables = 2

# literals = 4

$$= \overline{\overline{a}aa\overline{a}} \Rightarrow \text{# literals} = 4$$